

<<电路基础>>

图书基本信息

书名：<<电路基础>>

13位ISBN编号：9787030320124

10位ISBN编号：7030320123

出版时间：2011-8

出版时间：科学出版社

作者：（美）亚历山大 著

页数：924

版权说明：本站所提供下载的PDF图书仅提供预览和简介，请支持正版图书。

更多资源请访问：<http://www.tushu007.com>

## <<电路基础>>

### 内容概要

《电路基础(第四版)(英文影印版)》

讲述了电路课程的基础知识，分为三个部分：第一部分是直流电路，包括基本定律和定理、无源元件及有源元件。

第二部分是交流电路，包括相量、正弦稳态分析、功率、有效值、三相电路和频率响应。

第三部分包括拉普拉斯变换、傅里叶级数、傅里叶变换和二端口网络分析。

本书以电路的基础知识、分析方法为主体，并在此基础上适当地做了有创意的延伸与发展，加强了它与新技术的联系。

《电路基础(第四版)(英文影印版)》可作为电类各专业课程的双语教材或参考书，也可供工程技术人员参考。

## &lt;&lt;电路基础&gt;&gt;

## 书籍目录

preface xi
acknowledgments xvi
guided tour xviii
a note to the student xxiii
about the authors xxv
part 1 dc circuits 2
chapter 1 basic concepts 3
1.1 introduction 4
1.2 systems of units 4
1.3 charge and current 6
1.4 voltage 9
1.5 power and energy 10
1.6 circuit elements 15
1.7 *applications 17
1.8 *problem solving 20
1.9 summary 23
chapter 2 basic laws 29
2.1 introduction 30
2.2 ohm's law 30
2.3 *nodes, branches, and loops 35
2.4 kirchhoff's laws 37
2.5 series resistors and voltage division 43
2.6 parallel resistors and current division 45
2.7 *wye-delta transformations 52
2.8 *applications 58
2.9 summary 64
chapter 3 methods of analysis 81
3.1 introduction 82
3.2 nodal analysis 82
3.3 nodal analysis with voltage sources 88
3.4 mesh analysis 93
3.5 mesh analysis with current sources 98
3.6 *nodal and mesh analyses by inspection 100
3.7 nodal versus mesh analysis 104
3.8 circuit analysis with pspice 105
3.9 *applications: dc transistor circuits 107
3.10 summary 112
chapter 4 circuit theorems 127
4.1 introduction 128
4.2 linearity property 128
4.3 superposition 130
4.4 source transformation 135
4.5 thevenin's theorem 139
4.6 norton's theorem 145

## &lt;&lt;电路基础&gt;&gt;

- 4.7 \*derivations of thevenin's and norton's theorems 149
- 4.8 maximum power transfer 150
- 4.9 verifying circuit theorems with pspice 152
- 4.10 \*applications 155
- 4.11 summary 160
- chapter 5 operational amplifiers 175
- 5.1 introduction 176
- 5.2 operational amplifiers 176
- 5.3 ideal op amp 179
- 5.4 inverting amplifier 181
- 5.5 noninverting amplifier 183
- 5.6 summing amplifier 185
- 5.7 difference amplifier 187
- 5.8 cascaded opamp circuits 191
- 5.9 op amp circuit analysis with pspice 194
- 5.10 applications 196
- 5.11 summary 199
- chapter 6 capacitors and inductors 215
- 6.1 introduction 216
- 6.2 capacitors 216
- 6.3 series and parallel capacitors 222
- 6.4 inductors 226
- 6.5 series and parallel inductors 230
- 6.6 applications 233
- 6.7 summary 240
- chapter 7 first-order circuits 253
- 7.1 introduction 254
- 7.2 the source-free RC circuit 254
- 7.3 the source-free RL circuit 259
- 7.4 singularity functions 265
- 7.5 step response of an RC circuit 273
- 7.6 step response of an RL circuit 280
- 7.7 first-order op amp circuits 284
- 7.8 transient analysis with pspice 289
- 7.9 applications 293
- 7.10 summary 299
- chapter 8 second-order circuits 313
- 8.1 introduction 314
- 8.2 finding initial and final values 314
- 8.3 the source-free series RLC circuit 319
- 8.4 the source-free parallel RLC circuit 326
- 8.5 step response of a series RLC circuit 331
- 8.6 step response of a parallel RLC circuit 336
- 8.7 general second-order circuits 339
- 8.8 second-order op amp circuits 344
- 8.9 pspice analysis of RLC circuits 346
- 8.10 \*duality 350

## &lt;&lt;电路基础&gt;&gt;

- 8.11 applications 353
- 8.12 summary 356
- part 2 ac circuits 368
- chapter 11 sinusoids and phasors 369
- 9.1 introduction 370
- 9.2 sinusoids 371
- 9.3 phasors 376
- 9.4 phasor relationships for circuit elements 385
- 9.5 impedance and admittance 387
- 9.6 \*kirchhoff's laws in the frequency domain 389
- 9.7 impedance combinations 390
- 9.8 applications 396
- 9.9 summary 402
- chapter 10 sinusoidal steady-state analysis 413
- 10.1 introduction 414
- 10.2 nodal analysis 414
- 10.3 mesh analysis 417
- 10.4 superposition theorem 421
- 10.5 source transformation 424
- 10.6 thevenin and norton equivalent circuits 426
- 10.7 op amp ac circuits 431
- 10.8 ac analysis using pspice 433
- 10.9 applications 437
- 10.10 summary 441
- chapter 11 ac power analysis 457
- 11.1 introduction 458
- 11.2 instantaneous and average power 458
- 11.3 maximum average power transfer 464
- 11.4 effective or rms value 467
- 11.5 apparent power and power factor 470
- 11.6 complex power 473
- 11.7 conservation of ac power 477
- 11.8 power factor correction 481
- 11.9 applications 483
- 11.10 summary 488
- chapter 12 three-phase circuits 503
- 12.1 introduction 504
- 12.2 balanced three-phase voltages 505
- 12.3 balanced wye-wye connection 509
- 12.4 balanced wye-delta connection 512
- 12.5 balanced delta-delta connection 514
- 12.6 balanced delta-wye connection 516
- 12.7 power in a balanced system 519
- 12.8 unbalanced three-phase systems 525
- 12.9 pspice for three-phase circuits 529
- 12.10 applications 534
- 12.11 summary 543

## &lt;&lt;电路基础&gt;&gt;

- chapter 13 magnetically coupled circuits 555
  - 13.1 introduction 556
  - 13.2 mutual inductance 557
  - 13.3 energy in a coupled circuit 564
  - 13.4 linear transformers 567
  - 13.5 ideal transformers 573
  - 13.6 ideal autotransformers 581
  - 13.7 three-phase transformers 584
  - 13.8 pspice analysis of magnetically coupled circuits 586
  - 13.9 applications 591
  - 13.10 summary 597
- chapter 14 frequency response 613
  - 14.1 introduction 614
  - 14.2 transfer function 614
  - 14.3 the decibel scale 617
  - 14.4 bode plots 619
  - 14.5 series resonance 629
  - 14.6 parallel resonance 634
  - 14.7 passive filters 637
  - 14.8 active filters 642
  - 14.9 scaling 648
  - 14.10 frequency response using pspice 652
  - 14.11 computation using matlab 655
  - 14.12 applications 657
  - 14.13 summary 663
- part 3 advanced circuit analysis 674  
此处删去原书第15.16章。
  
- chapter 17 the fourier series 755
  - 17.1 introduction 756
  - 17.2 trigonometric fourier series 756
  - 17.3 symmetry considerations 764
  - 17.4 circuit applications 774
  - 17.5 average power and rms values 778
  - 17.6 exponential fourier series 781
  - 17.7 fourier analysis with pspice 787
  - 17.8 applications 793
  - 17.9 summary 796
- 此处删去原书第18章。
  
- chapter 19 two-port networks 849
  - 19.1 introduction 850
  - 19.2 impedance parameters 850
  - 19.3 admittance parameters 855
  - 19.4 hybrid parameters 858
  - 19.5 transmission parameters 863
  - 19.6 relationships between

<<电路基础>>

- 19.7 interconnection of networks 871
- 19.8 computing two-port parameters using pspice 877
- 19.9 applications 880
- 19.10 summary 889
- appendix a simultaneous equations and matrix inversion a
- appendix b complex numbers a-9
- appendix c mathematical formulas a-16
- appendix d pspice for windows a-91
- appendix e matlab a-46
- appendix f kcide for circuits a-65
- appendix g answers to odd-numbered problems a-75
- bibliography b-1

<<电路基础>>

版权说明

本站所提供下载的PDF图书仅提供预览和简介，请支持正版图书。

更多资源请访问:<http://www.tushu007.com>